


ADUM2402
iCoupler

LTC4260
Hot Swap
Controller

Power entry

DC/DC converter

Switching FET

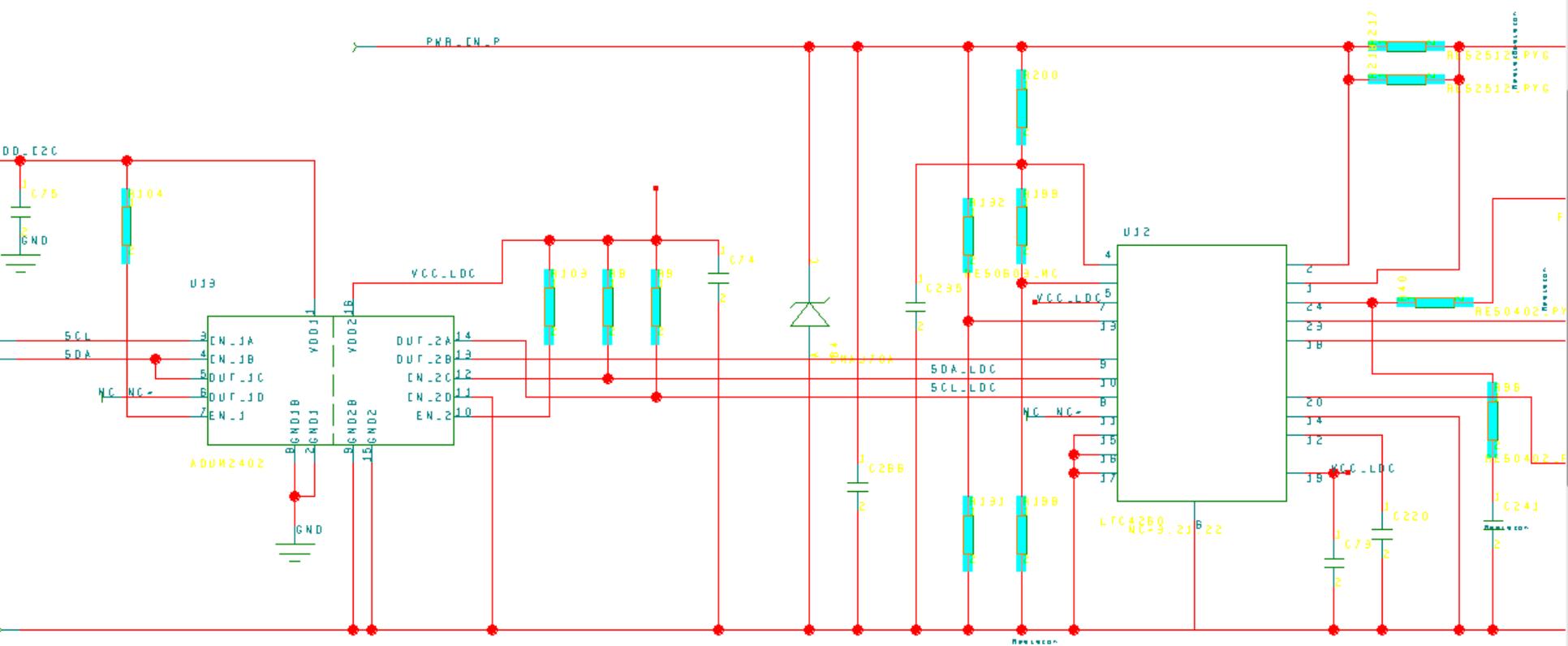


ADIN can be used to measure the input supply

$$ADIN = (1.5 / (56.2 + 1.5)) \times V_{in} = 0.026 \times V_{in} \quad (V_{in} = 48V \rightarrow A_{din} = 1.25V)$$

- Sensitive isolated power input.
After a spike on the 48V power supply (e.g. hot unplug board) the hot-swap controller is blocked... board has no power.

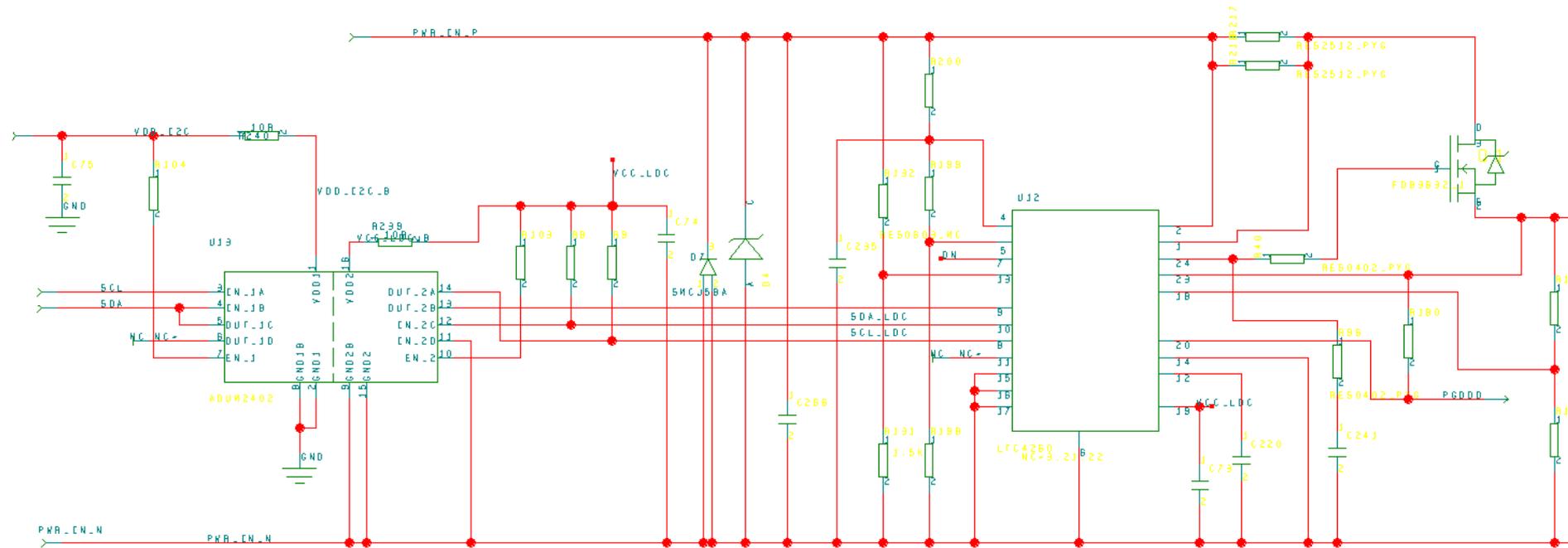- More measurements have been done....
- The spike on the input ripples through the HotSwap controller to the power of the ADUM2402 (iCoupler) which breaks the iCoupler and this in turn blocks the hot swap controller.
- By Replacing the ADUM the error is solved.
- For new release the schematic is adjusted..



ADIN can be used to measure the input supply
 $ADIN = (1.5 / (56.2 + 1.5)) \times V_{in} = 0.026 \times V_{in}$ ($V_{in} = 48V \rightarrow ADIN = 1.25V$)

- 10E resistor on power supplies to iCoupler
- Elco on power supply iCoupler
- Extra zenerdiode on 48V input
- Extra diode on 48V input.